

## Fall-2021 UM-SJTU JI Ve311 Homework #2

Instructor: Dr. Chang-Ching Tu


Due: 10:40 am, October 13, 2021 (Wednesday), online submission

Note:

- (1) Please use A4 size papers.
- (2) Please use the SPICE model below for simulation.

```
.model Dbreak D Is=1e-10 Rs=0 N=1 TT=0 Cjo=0pF
```

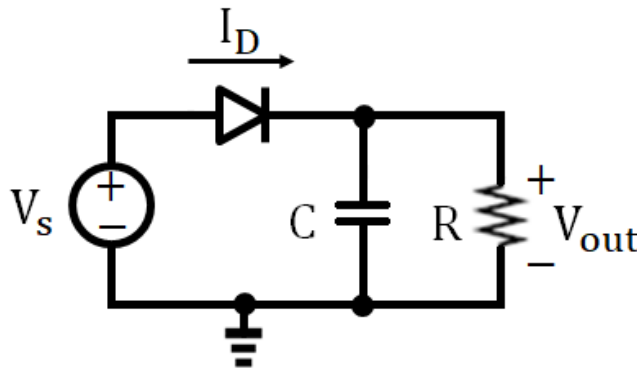1. [Half-Wave Rectifier] Design a half-wave rectifier circuit, such as below, which can convert a sinusoidal voltage input,  $V_s = 5\sin(2\pi 100 \cdot \text{time})$ , to an almost constant voltage output.
  - (a) [20%] Assuming  $V_{on} = 0.9 \text{ V}$  and  $R = 100 \Omega$ , calculate  $C$  which makes the ripple voltage ( $V_r$ ) is smaller than  $0.1 \text{ V}$ . Estimate  $V_{dc}$ ,  $I_{dc}$ ,  $\theta_c$ ,  $\Delta T$ ,  $I_{peak}$ ,  $I_{surge}$  and PIV of the designed half-wave rectifier.
  - (b) [15%] Based on the calculated  $C$ , in Pspice plot  $V_s$  and  $V_{out}$  versus time on the sample graph to find out the values of  $V_{dc}$ ,  $I_{dc}$ ,  $V_r$  and PIV. Compare the simulation results with the hand-calculated ones.
  - (c) [15%] In Pspice, plot  $I_D$  versus time to find out the values of  $I_{peak}$  and  $I_{surge}$ . Compare the simulation results with the hand-calculated ones.



2. [Full-Wave Bridge Rectifier] Design a full-wave bridge rectifier circuit, such as below, which can convert a sinusoidal voltage input,  $V_s = 5\sin(2\pi 100 \cdot \text{time})$ , to an almost constant voltage output.
- [20%] Assuming  $V_{on} = 0.9 \text{ V}$  and  $R = 100 \Omega$ , calculate  $C$  which makes the ripple voltage ( $V_r$ ) smaller than  $0.1 \text{ V}$ . Estimate  $V_{dc}$ ,  $I_{dc}$ ,  $\theta_c$ ,  $\Delta T$ ,  $I_{peak}$ ,  $I_{surge}$  and PIV of the designed full-wave bridge rectifier.
  - [15%] Based on the calculated  $C$ , in Pspice plot  $V_s$  (using “voltage differential marker” function) and  $V_{out}$  versus time on the sample graph to find out the values of  $V_{dc}$ ,  $I_{dc}$ ,  $V_r$  and PIV. Compare the simulation results with the hand-calculated ones.
  - [15%] In Pspice, plot  $I_{D2}$  and  $I_{D3}$  versus time on the same graph to find out the values of  $I_{peak}$  and  $I_{surge}$ . Compare the simulation results with the hand-calculated ones.

