



JOINT INSTITUTE

交大密西根学院

BJT and BJT Circuit


Ve311 Electronic Circuits (Fall 2021)

Dr. Chang-Ching Tu

BJT (Before Contact)

Emitter

n-type

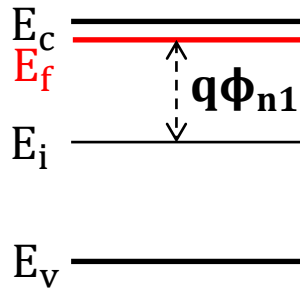


$$n \cong N_{d1} = n_i e^{\frac{q\phi_{n1}}{kT}}$$

$$p \cong \frac{n_i^2}{N_{d1}} = n_i e^{\frac{-q\phi_{n1}}{kT}}$$

Base

p-type

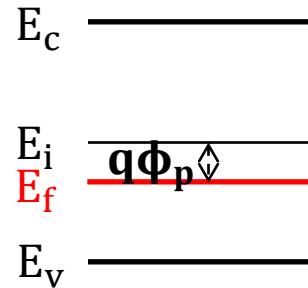


$$p \cong N_a = n_i e^{\frac{q\phi_p}{kT}}$$

$$n \cong \frac{n_i^2}{N_a} = n_i e^{\frac{-q\phi_p}{kT}}$$

Collector

n-type

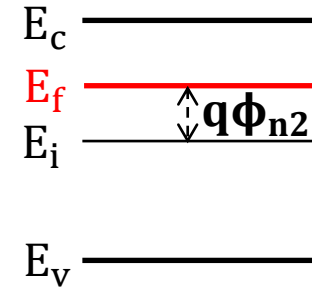


$$n \cong N_{d2} = n_i e^{\frac{q\phi_{n2}}{kT}}$$

$$p \cong \frac{n_i^2}{N_{d2}} = n_i e^{\frac{-q\phi_{n2}}{kT}}$$

$$N_{d1} \gg N_a$$

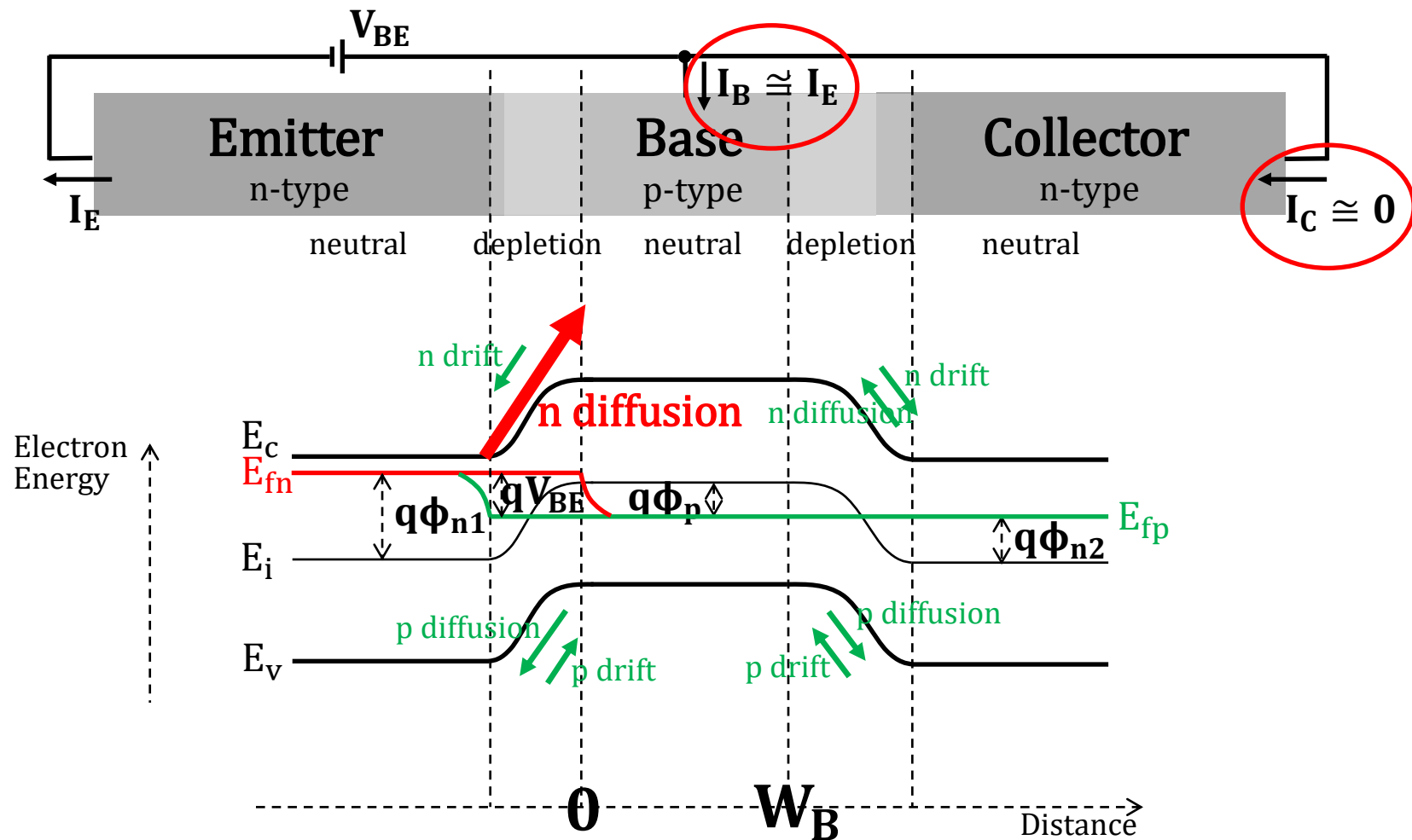
$$V_{BE} > 0 \text{ and } V_{CB} = 0 \text{ (} W_B \text{ long)}$$



$$N_{d1} \gg N_a$$

The n (electron) diffusion is much larger than the p (hole) diffusion at the Base-Emitter junction.

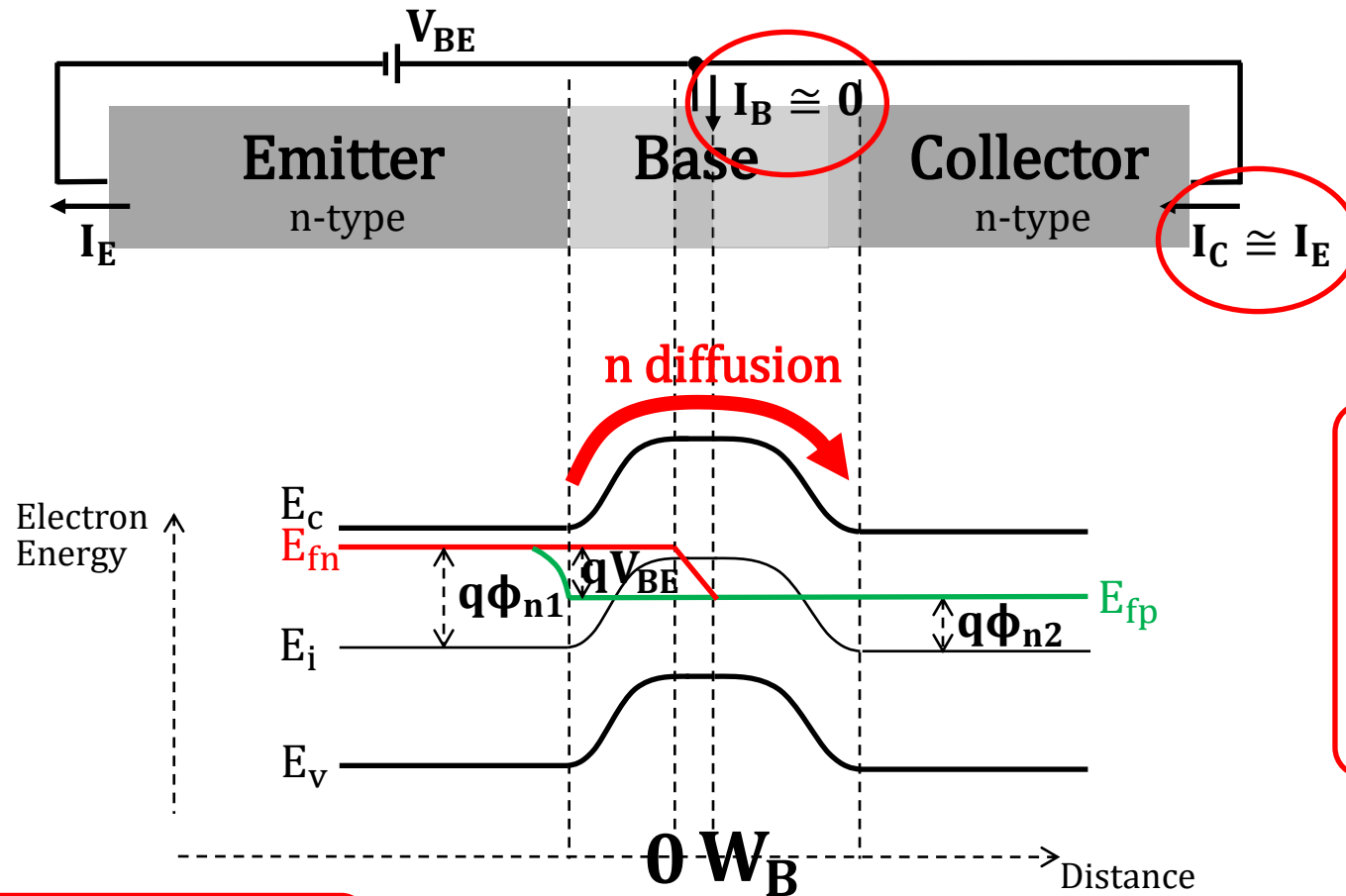$V_{BE} > 0$ and $V_{CB} = 0$ (W_B very short)



$$I_E = I_C + I_B$$

$$\frac{I_C}{I_E} = \alpha$$

$$\frac{I_C}{I_B} = \beta$$


$$N_{d1} \gg N_a$$

The n (electron) diffusion is much larger than the p (hole) diffusion at the Base-Emitter junction.

W_B very short

Nearly all the n (electron) diffusion from the Base-Emitter junction pass through the Base, enter into the depletion region of the Base-Collector junction, and are swept to the Collector side by the built-in electric field.

Summary

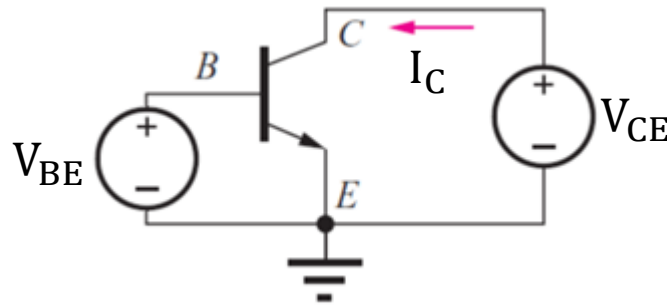

$V_{CE} \geq V_{BE}$
 \Rightarrow Forward – Active

Ideal case

$$I_C = I_S \left(e^{\frac{qV_{BE}}{kT}} - 1 \right)$$

$$\alpha = \frac{I_C}{I_E} \cong 1$$

$$\beta = \frac{I_C}{I_B} = \frac{\alpha}{1 - \alpha}$$



$$I_C = I_S \left(e^{\frac{qV_{BE}}{kT}} - 1 \right)$$

$$\alpha = \frac{I_C}{I_E} = 1$$

$$\beta = \frac{I_C}{I_B} = \infty$$



I_S is a constant in the spice model.

I_C vs V_{CE} and I_C vs V_{BE}
in Forward-Active Region

I_C vs V_{CE} (not considering Early Effect)



7

At given V_{BE} , DC sweep V_{CE}

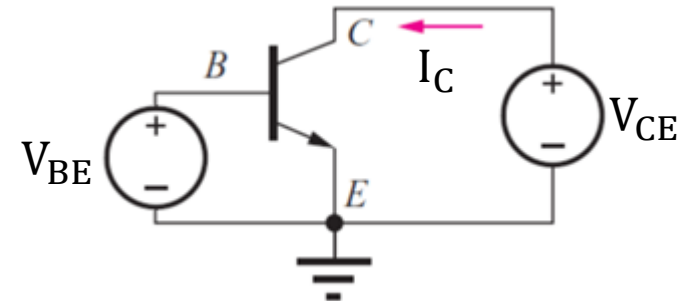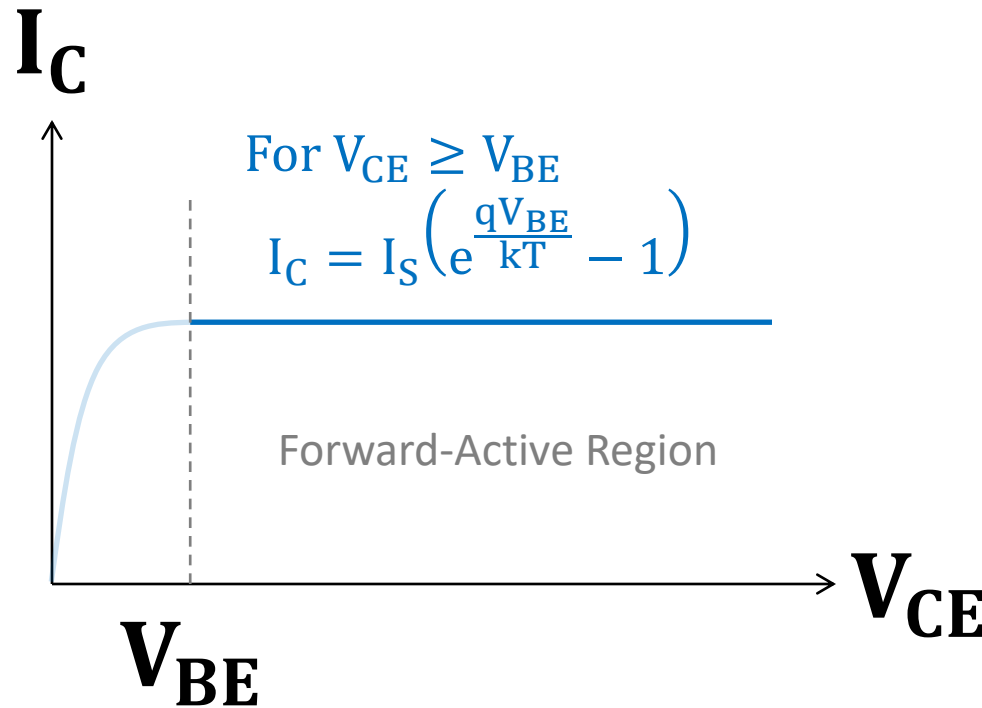

I_C vs V_{CE} (considering Early Effect)

At given V_{BE} , DC sweep V_{CE}

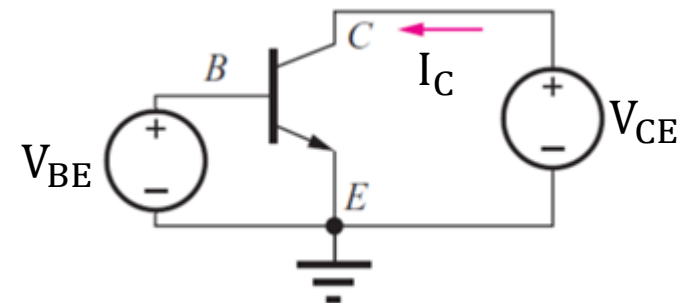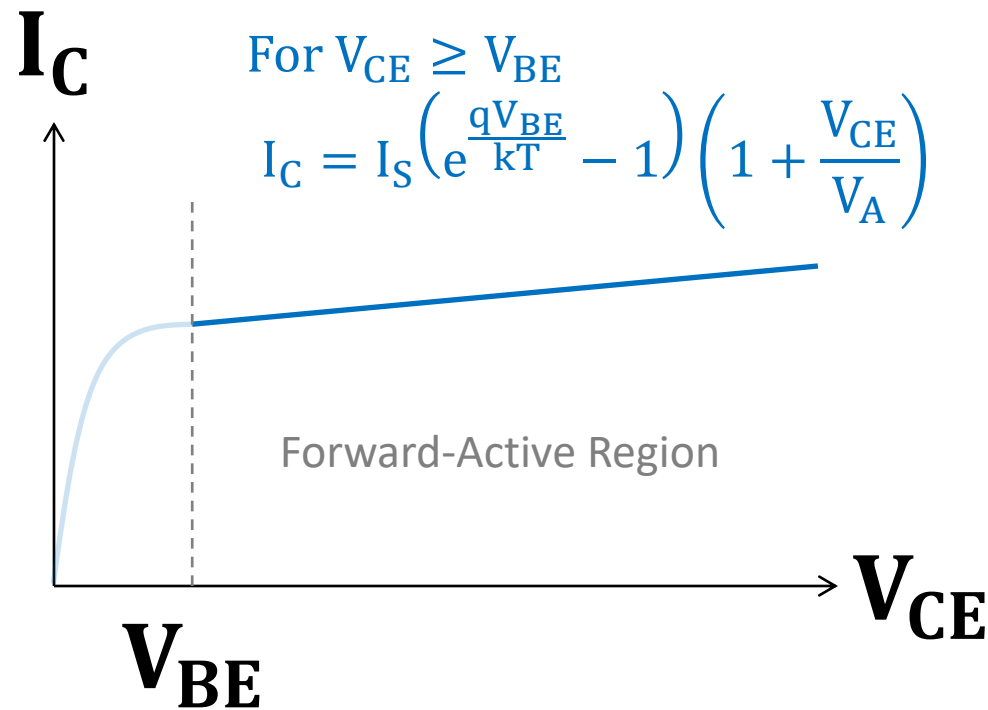



V_A is a constant in the spice model.

I_C vs V_{BE}

At given V_{CE} , DC sweep V_{BE}

For $V_{CE} \geq V_{BE}$

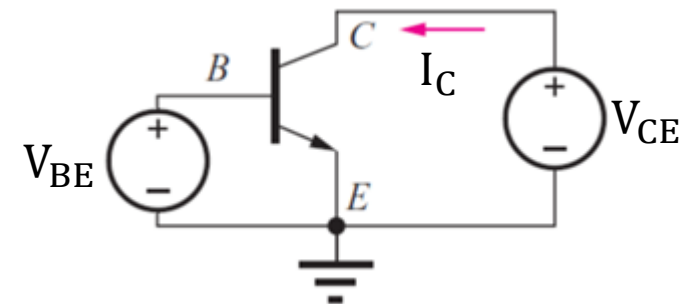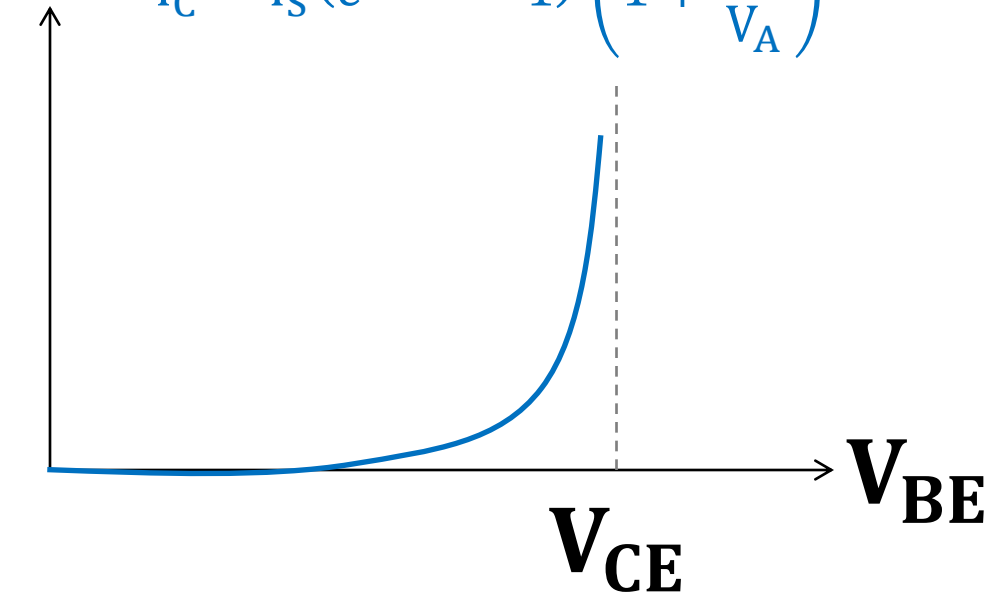
$$I_C = I_S \left(e^{\frac{qV_{BE}}{kT}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$



Small-Signal Model

Hybrid- π Model (how to get g_m and r_π)

Complete circuit:

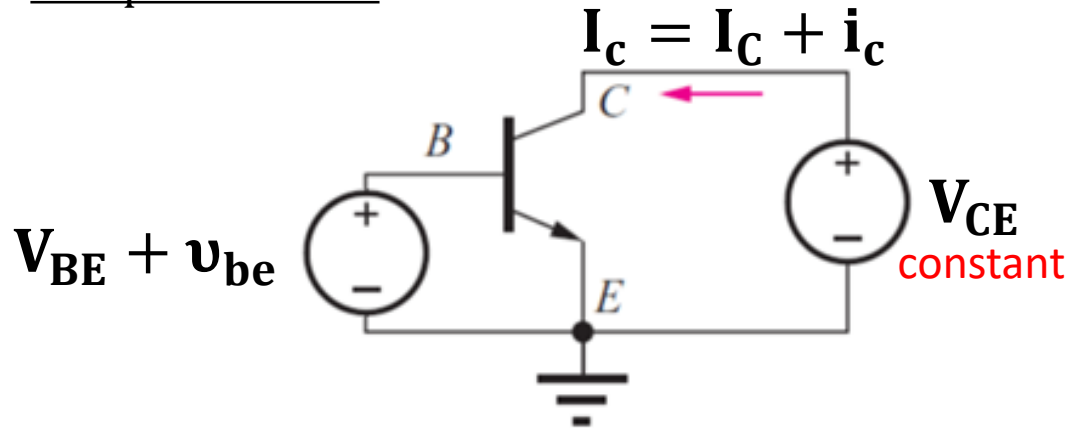


$$V_{CE} \geq V_{BE}$$

\Rightarrow Forward – Active

$$I_C = I_S \left(e^{\frac{qV_{BE}}{kT}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$



Small-signal circuit:

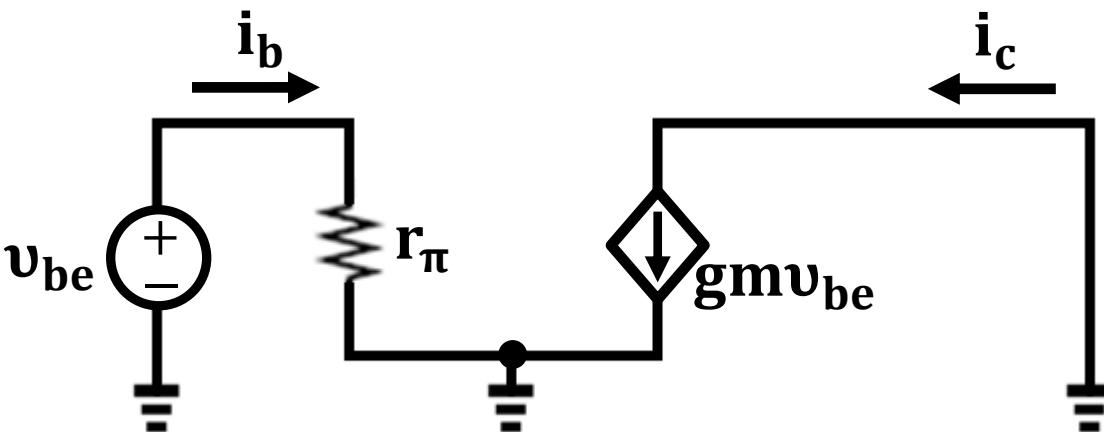


$$r_\pi = \frac{dV_{BE}}{dI_B} = \frac{1}{\frac{dI_C}{\beta dV_{BE}}} = \frac{1}{\frac{g_m}{\beta}} = \frac{\beta}{g_m}$$

$$g_m = \frac{dI_C}{dV_{BE}} \cong \frac{I_C}{kT/q}$$

Hybrid- π Model (how to get r_o)

Complete circuit:

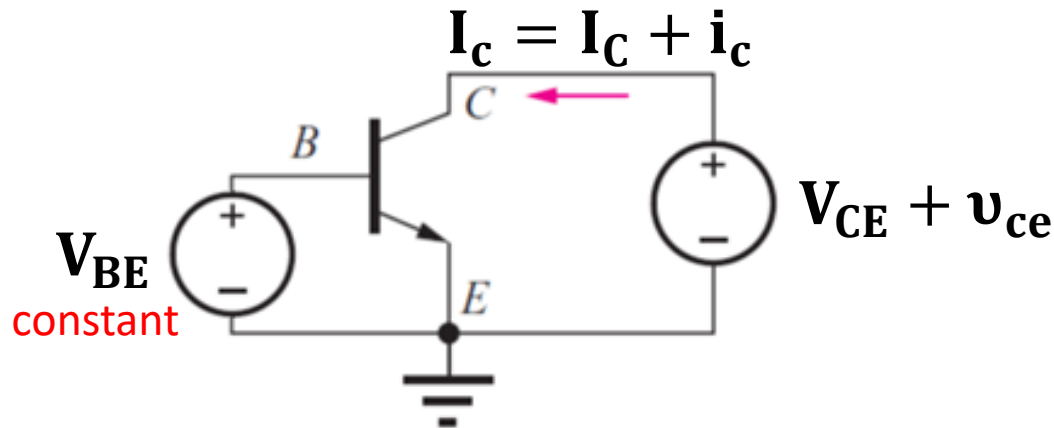


$$V_{CE} \geq V_{BE}$$

\Rightarrow Forward – Active

$$I_C = I_S \left(e^{\frac{qV_{BE}}{kT}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$



Small-signal circuit:

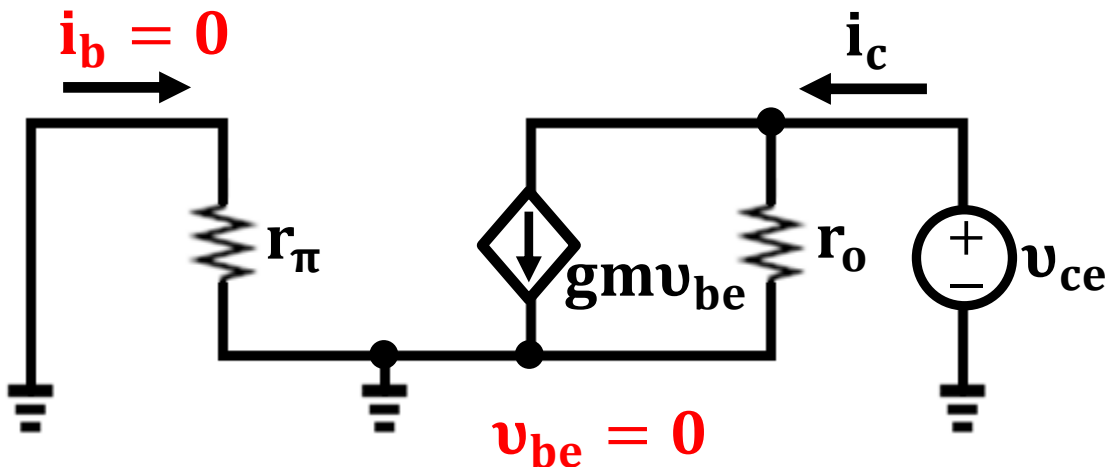


$$r_\pi = \frac{1}{\frac{dI_B}{dV_{BE}}} = \frac{1}{\frac{dI_C}{\beta dV_{BE}}} = \frac{1}{\frac{gm}{\beta}} = \frac{\beta}{gm}$$

$$gm = \frac{dI_C}{dV_{BE}} \approx \frac{I_C}{kT/q}$$

$$r_o = \frac{1}{\frac{dI_C}{dV_{CE}}} \approx \frac{V_A}{I_C}$$

Common-Emitter Amplifier

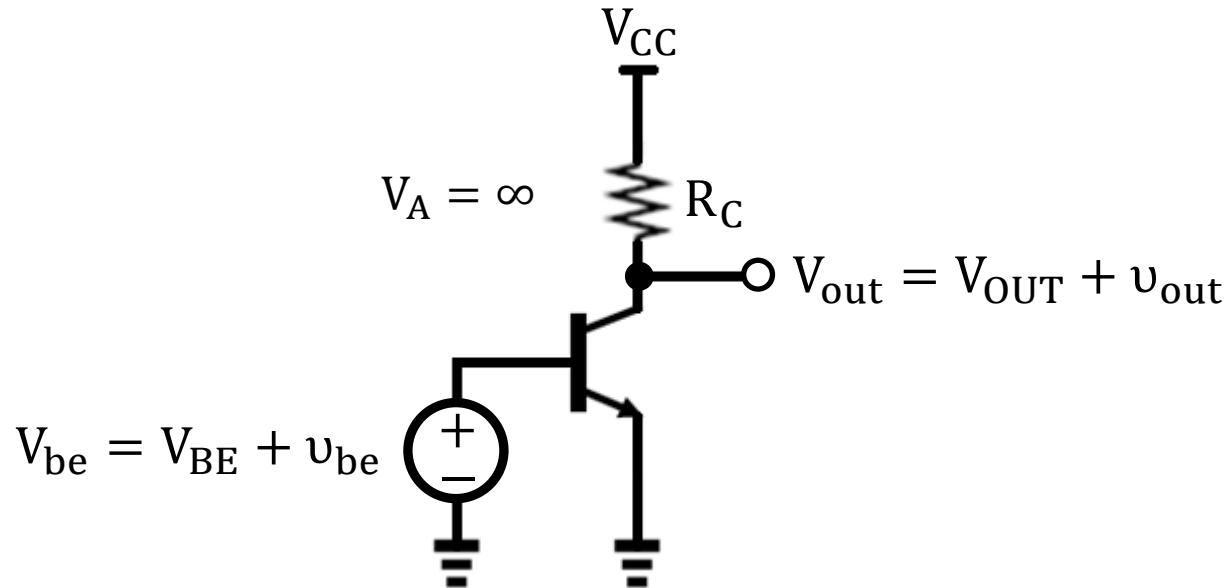Common-Emitter Amplifier ($V_A = \infty$)




• DC Analysis


$$V_{OUT} = V_{CC} - I_C R_C$$

$$= V_{CC} - \frac{A q D_n n_i^2}{N_a W_B} \left(e^{\frac{q V_{BE}}{k T}} - 1 \right) R_C$$

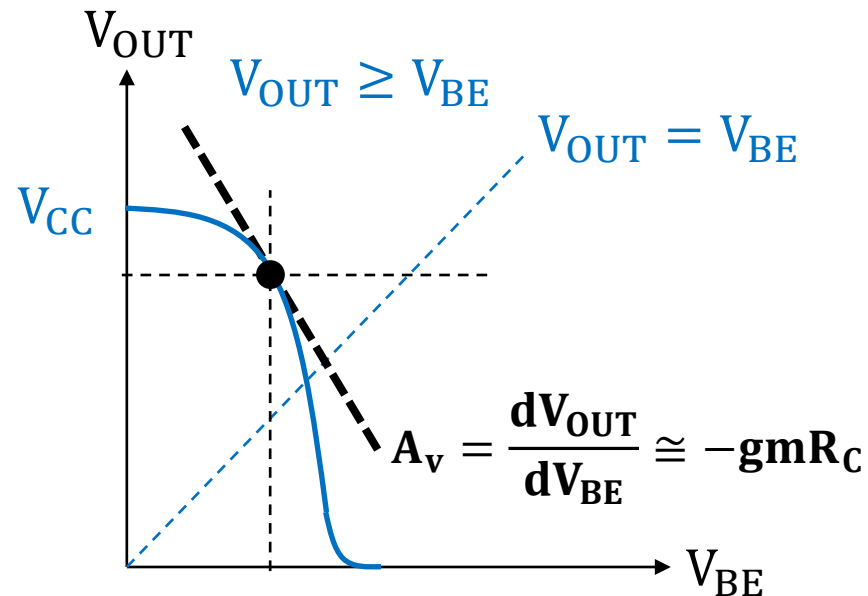
$$A_v = \frac{dV_{OUT}}{dV_{BE}} \cong -\frac{I_C}{kT/q} R_C = -g_m R_C$$



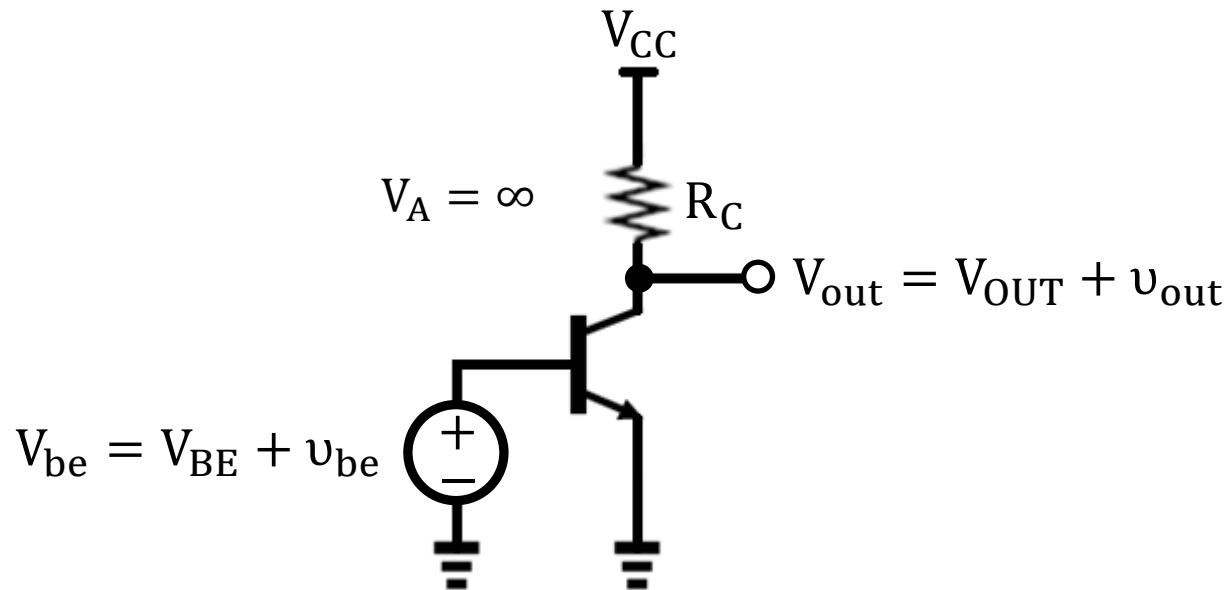Common-Emitter Amplifier ($V_A = \infty$)




- Small-Signal Analysis

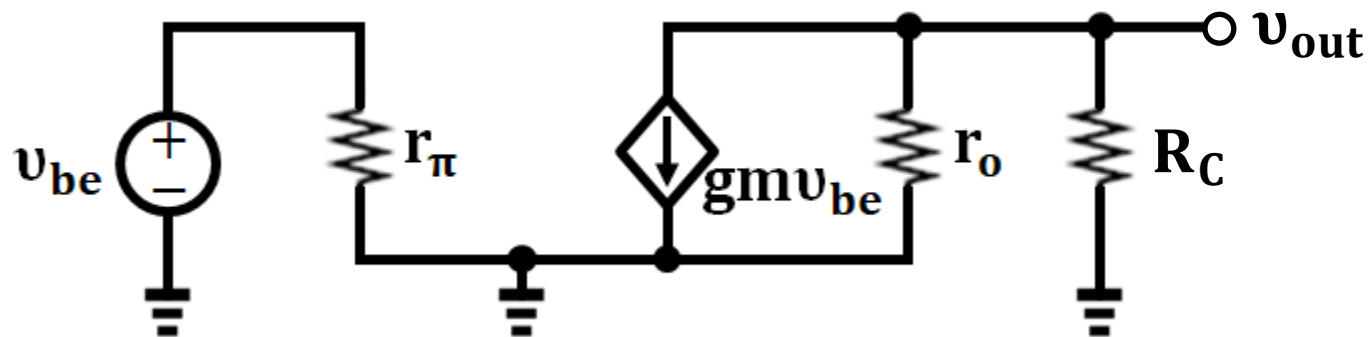

$$A_v = \frac{v_{out}}{v_{be}} = -gm(R_C \parallel r_o) = -gmR_C \quad (\text{since } r_o = \infty)$$

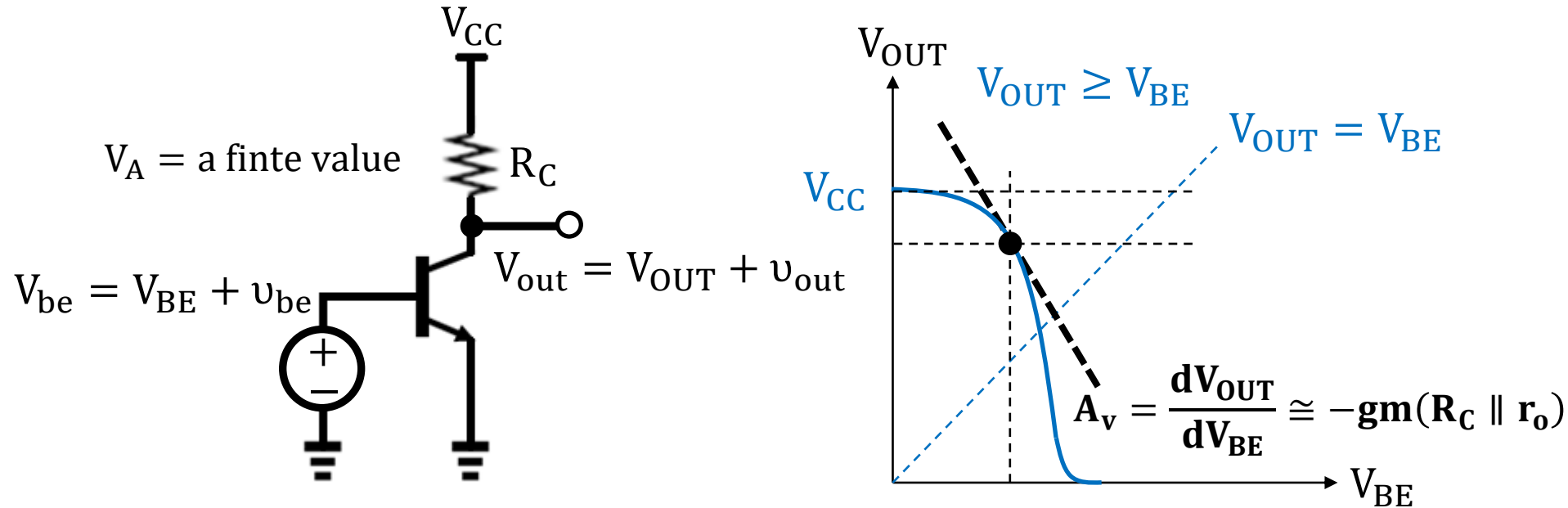Common-Emitter Amplifier ($V_A = \text{a finite value}$)¹⁶




• DC Analysis

$$V_{OUT} = V_{CC} - I_C R_C = V_{CC} - I_S \left(e^{\frac{qV_{BE}}{kT}} - 1 \right) \left(1 + \frac{V_{OUT}}{V_A} \right) R_C$$


$$\frac{dV_{OUT}}{dV_{BE}} = -\frac{q}{kT} I_S e^{\frac{qV_{BE}}{kT}} \left(1 + \frac{V_{OUT}}{V_A} \right) R_C - I_S \left(e^{\frac{qV_{BE}}{kT}} - 1 \right) \frac{1}{V_A} \frac{dV_{OUT}}{dV_{BE}} R_C \cong -gm R_C - \frac{1}{r_o} \frac{dV_{OUT}}{dV_{BE}} R_C$$

$$A_v = \frac{dV_{OUT}}{dV_{BE}} \cong -gm(R_C \parallel r_o)$$

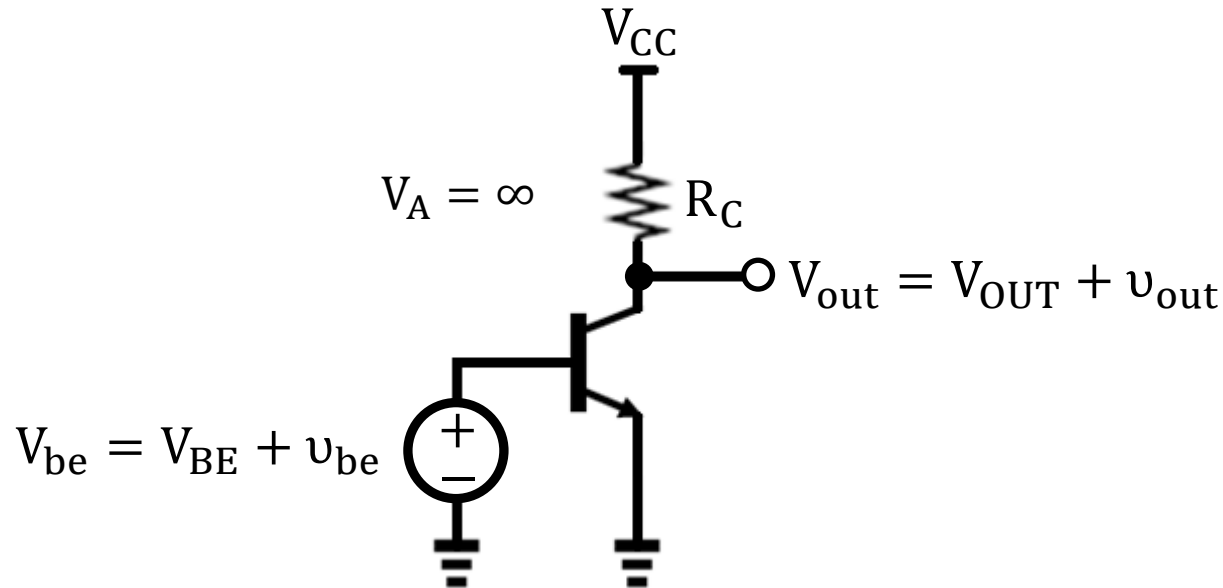Common-Emitter Amplifier ($V_A = \text{a finite value}$)¹⁷




- Small-Signal Analysis

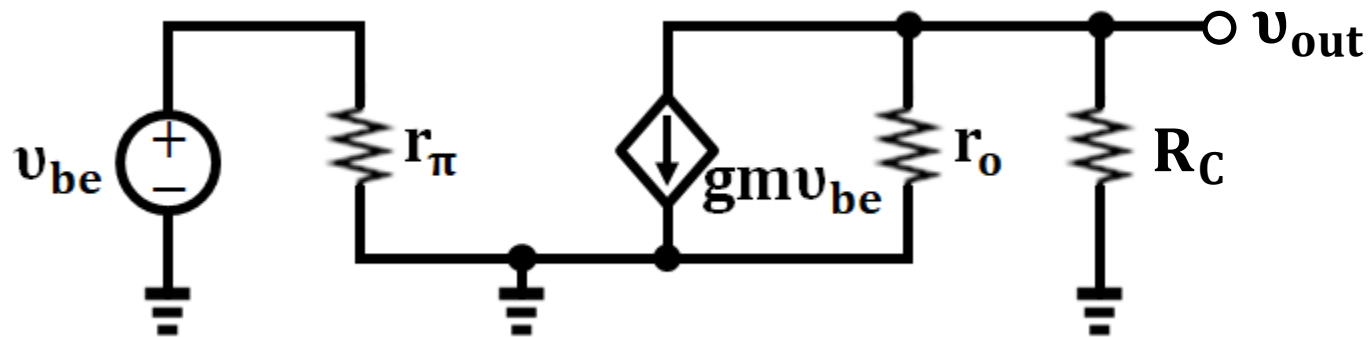

$$A_v = \frac{v_{out}}{v_{be}} = -gm(R_C \parallel r_o)$$

BJT Structure and Pspice Model

nnp BJT Cross Section

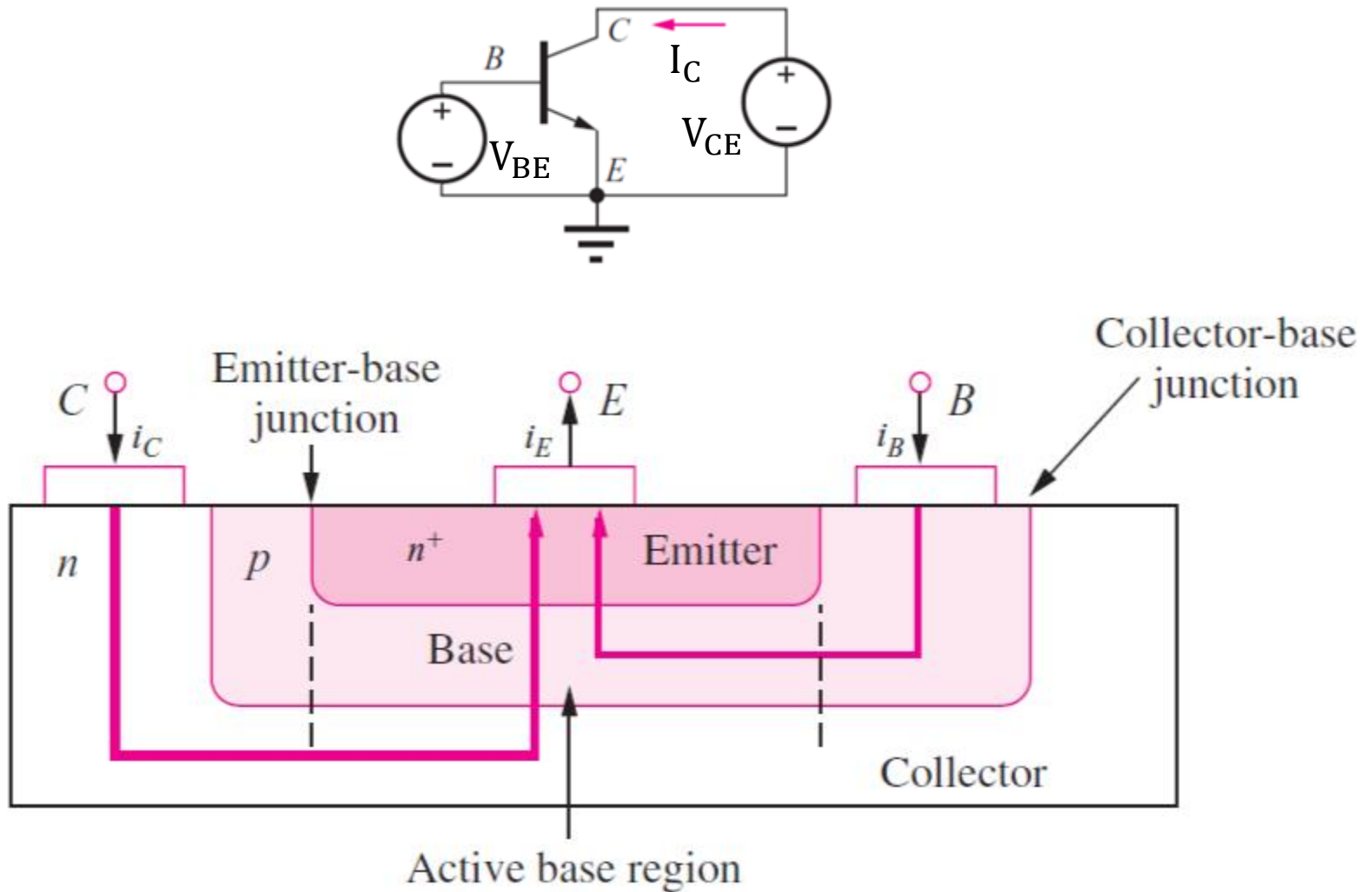

npn BJT Pspice Model

.model Qbreakn NPN IS=1e-18 BF=100 VAF=100

$$I_C = \textcolor{blue}{IS} \left(e^{\frac{qV_{BE}}{kT}} - 1 \right) \left(1 + \frac{V_{CE}}{\textcolor{blue}{VAF}} \right)$$

$$\textcolor{blue}{BF} = \frac{I_C}{I_B} \quad I_E = I_C + I_B$$

$$gm \cong \frac{I_C}{kT/q} \quad r_\pi = \frac{\textcolor{blue}{BF}}{gm} \quad r_o \cong \frac{\textcolor{blue}{VAF}}{I_C}$$